

## Lab # 04 Task

- 1) Reduce the following Boolean functions using K-Map. Make the truth table for the reduced expression and then simulate the simplified/reduced expression on Logicly.

I.  $F = A'B + AB' + AB$

II.  $F = A'B'C + A'BC + ABC' + ABC$

- 2) Identify the Minterm and Maxterm for the following truth table.

S.no	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

- 3) Simplify the following Boolean functions using K-Map.

I.  $F(A,B) = \sum (2,3)$

II.  $F(A,B,C) = \sum (2,3,6,7)$

III.  $F(A,B,C,D) = \sum (0,2,5,7,8,10,14,15)$

IV.  $F(A, B, C, D) = \sum (0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$