

EL227- Digital Logic Design Lab

Lab # 10 BCD to 7 Segment Display

- Use **Multism** to design circuit diagrams.
 - Label your inputs and outputs properly on logic.ly
-
1. Design 7 segment decoder circuit to display the following digits on 7 segment display.
(3, 5, 9).
 2. Test the functionality of a 8x1 multiplexer using the IC-74LS151
 3. Test the functionality of a 4x1 multiplexer using the IC-74LS153
 4. Implement the following Boolean functions on Multism using the AND, OR, NOT IC's.
$$F=A'.B + A.B'$$
$$F=A'.B' + A.B$$