

Lab # 08 Encoder and Decoder Task

- Use **Logic.ly** to design circuit diagrams.
 - Label your inputs and outputs properly on logic.ly
-
1. Design the circuitry for Octal to Binary Encoder.
 2. Implement the circuitry for a Decimal to BCD Encoder.
 3. Implement the circuitry for 3x8 decoder.
 4. Design an 8x3 Encoder using NAND Gates only.
 5. Implement full-Adder using 3x8 Decoder.
 6. Implement full-subtractor using 3x8 Decoder.