

Lab # 06 Task

1. Design and implement the circuitry for a Half subtractor and simulate it on Logically.
2. Implement a half subtractor using AND, OR and NOT gates only and simulate it on Logically.
3. Design and implement the circuitry of a full subtractor and simulate it on Logically.
4. Implement the half subtractor using NOR Gates only and simulate it on Logically.
5. Implement the full subtractor using NOR Gates only and simulate it on Logically.
6. Design and implement the circuitry for 2 bit binary number subtraction on Logically.

Subtract the following two bit binary numbers on Logically.

A = 11, B = 10

7. Write the Boolean expression for Difference (A-B-C) and Borrow (C') that describe the below truth table by simplifying using k-maps.

Inputs			Output	
A	B	C	(A-B-C)	C'
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

8. Design and implement the circuitry for a BCD-to-Excess 3 Code Converter.